



# **A Project Report**


**on**

## **16 Bit RISC Processor**

Created By -

Anirban Nath

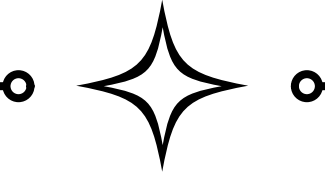[anirbannath3@gmail.com](mailto:anirbannath3@gmail.com)



# 16 Bit RISC Processor

## Design

### ALU

```
`timescale 1ns / 1ps

//module declarations
module alu(

    //input declarartion
    input I_clk,
    input I_en,
    input [4:0] I_aluop,
    input [15:0] I_dataA,
    input [15:0] I_dataB,
    input [7:0] I Imm,

    //output declarartion
    output [15:0] O_dataResult,
    output reg O_shldBranch
);

//reg/wire declarartion
reg [17:0] int_result;
wire [3:0] opcode;
wire op_lsb

//initial block
initial
    int_result <=0;

//assign values
assign op_lsb = I_aluop[0];
assign opcode = I_aluop[4:1];

//parameter declaration
localparam add=0,
    sub=1,
    or1 = 2,
    and1 =3,
    xor1 =4,
    not1 =5,
    load=8,
    cmp=9, //compare
    shl=10, //shift by left
    shr=11, //shift by right
    jmpa=12, //jump address
    jmpr=13; //jump resgiter

//ALU operations
always @(negedge I_clk) begin

    if(I_en) begin

        case(opcode)

            add : begin
                int_result <= (op_lsb ? ($signed(I_dataA) + $signed(I_dataB))
                : (I_dataA) + (I_dataB));
                O_shldBranch <=0;
            end

            sub : begin
                int_result <= (op_lsb ? ($signed(I_dataA) - $signed(I_dataB))
                : (I_dataA) - (I_dataB));
                O_shldBranch <=0;
            end

            or1 : begin
                int_result <= I_dataA | I_dataB;
                O_shldBranch <=0;
            end

            and1 : begin
                int_result <= I_dataA & I_dataB;
                O_shldBranch <=0;
            end

            xor1 : begin
                int_result <= I_dataA ^ I_dataB;
                O_shldBranch <=0;
            end

            not1 : begin
                int_result <= ~I_dataA;
                O_shldBranch <=0;
            end

            load : begin
                int_result <= (op_lsb ? {I Imm, 8'h00} : {8'h00, I Imm});
                O_shldBranch <=0;
            end

        endcase
    end
end
```

```

cmp : begin

    if(op_lsb) begin
        int_result[0] <= ($signed(I_dataA) == $signed(I_dataA)) ? 1:0;
        int_result[1] <= ($signed(I_dataA) == 0) ? 1:0;
        int_result[2] <= ($signed(I_dataB) == 0) ? 1:0;
        int_result[3] <= ($signed(I_dataA) > $signed(I_dataB)) ? 1:0;
        int_result[4] <= ($signed(I_dataA) < $signed(I_dataB)) ? 1:0;
        O_shldBranch <= 0;
    end

    else begin
        int_result[0] <= ($signed(I_dataA) == $signed(I_dataA)) ? 1:0;
        int_result[1] <= ($signed(I_dataA) == 0) ? 1:0;
        int_result[2] <= ($signed(I_dataB) == 0) ? 1:0;
        int_result[3] <= ($signed(I_dataA) > $signed(I_dataB)) ? 1:0;
        int_result[4] <= ($signed(I_dataA) < $signed(I_dataB)) ? 1:0;
        O_shldBranch <= 0;
    end

    shl : begin
        int_result <= I_dataA << (I_dataB[3:0]);
        O_shldBranch <= 0;
    end

    shl : begin
        int_result <= I_dataA >> (I_dataB[3:0]);
        O_shldBranch <= 0;
    end

    jmpa : begin
        int_result <= (op_lsb ? I_dataA : I_imm );
        O_shldBranch <= 1;
    end

    /*jmpr : begin
        int_result <= I_dataA;
        O_shldBranch <= I_dataB [op_lsb,I_imm[1:0]];

    end */

    endcase

end

end

endmodule

```

## Instruction Decoder

```
`timescale 1ns/1ps

//module instruction decoder
module Inst_Dec(

    //input declaration
    input I_clk,
    input I_en,
    input [15:0] I_inst,

    //output declaration
    output reg [4:0] O_aluop,
    output reg [3:0] O_selA,
    output reg [3:0] O_selB,
    output reg [3:0] O_selD,
    output reg O_regwe,
    output reg O_imm

);

    //initial Block
    initial begin
        O_aluop <=0;
        O_selA <=0;
        O_selB <=0;
        O_selD <=0;
        O_imm <=0;
        O_regwe <=0;
    end

    always @(negedge I_clk) begin
        if(I_en) begin
            O_aluop <= I_inst [15:11]; //OPCODE
            O_selA <= I_inst [10:8]; //REG A
            O_selB <= I_inst [7:5]; //REG B
            O_selD <= I_inst [4:2]; //REG D
            O_imm <= I_inst [7:0]; // IMM DATA

            case (I_inst [15:12])

                4'b0111 : O_regwe<=0;
                4'b1100 : O_regwe<=0;
                4'b1101 : O_regwe<=0;
                default : O_regwe<=1;
            endcase
        end
    end

endmodule
```

## Control Unit

```
`timescale 1ns/1ps

module cntrl_unit(

    //input declaration
    input I_clk,
    input I_reset,

    //output declaration
    output O_enfetch,
    output O_endec,
    output O_enrgdr,
    output O_enrgwr,
    output O_enu,
    output O_enmem
);

    reg [5:0] state; //reg declaration

    initial begin
        state <=6'b000001;
    end

    always @(posedge I_clk) begin
        if(I_reset)
            state <=6'b000001;
        else begin
            case (state)
                6'b000001 : state<=6'b000010;
                6'b000010 : state<=6'b000100;
                6'b000100 : state<=6'b001000;
                6'b001000 : state<=6'b010000;
                6'b010000 : state<=6'b100000;
            endcase
        end
    end

    assign O_enfetch =state [0];
    assign O_endec =state [1];
    assign O_enrgdr =state [2];
    assign O_enu =state [3];
    assign O_enrgwr =state [4];
    assign o_enmem =state [5];

endmodule
```

# RAM

```
`timescale 1ns/1ps

//module declarations
module fake_RAM(
    //input declarations
    input I_clk,
    input I_we,
    input [15:0] I_addr,
    input [15:0] I_data,

    //output
    output [15:0] O_data
);

//memory declarations
reg [15:0] mem [8:0];
reg [15:0] O_data;

//initialize registers
initial begin

    mem[0]=16'b10000000011111110;
    mem[1]=16'b1000100111101101;
    mem[2]=16'b0010001000100000;
    mem[3]=16'b1000000001111111;
    mem[4]=16'b1100000000011110;
    mem[5]=16'b1010000001100110;
    mem[6]=16'b1000000111111110;
    mem[7]=0;
    mem[8]=0;

    O_data =16'b0000000000000000;
end

//RAM operations
always @(negedge I_clk) begin

    if(I_we) begin
        mem[I_addr [15:0]] <=I_data;
    end

    O_data<= mem[I_addr [15:0]];
end

endmodule
```

# Program Counter

```
`timescale 1ns/1ps

//module definition
module pc_unit(

    //input
    input I_clk,
    input [1:0] I_opcode,
    input [15:0] I_pc,

    //output
    output reg [15:0] O_pc
);

//initial block
initial begin
    O_pc<=0;
end

//Program counter state
always @(negedge I_clk) begin

    case (I_opcode)
        2'b00 : O_pc <=O_pc;
        2'b01 : O_pc <=O_pc+1;
        2'b10 : O_pc <=I_pc;
        2'b11 : O_pc <=0;
    endcase

end

endmodule
```

# Register Handler

```
`timescale 1ns/1ps

// Register File Module
module reg_file(
    input I_clk,
    input I_en,
    input I_we,
    input [2:0] I_selA,
    input [2:0] I_selB,
    input [2:0] I_selD,
    input [15:0] I_dataD,
    output reg [15:0] O_dataA,
    output reg [15:0] O_dataB
);

    reg [15:0] regs [7:0];
    integer count;

    initial begin
        O_dataA = 0;
        O_dataB = 0;
        for (count = 0; count < 8; count = count + 1) begin
            regs[count] = 0;
        end
    end

    always @(negedge I_clk) begin
        if (I_en) begin
            if (I_we)
                regs[I_selD] <= I_dataD;
            O_dataA <= regs[I_selA];
            O_dataB <= regs[I_selB];
        end
    end

endmodule
```

# Testbench

## Decoder UUT

```
`timescale 1ns/1ps
```

```
// Instruction Decoder Unit Testbench
```

```
module inst_dec_unittest();
```

```
    reg I_clk;
```

```
    reg I_en;
```

```
    reg [15:0] I_inst;
```

```
    wire [4:0] O_aluop;
```

```
    wire [2:0] O_selA;
```

```
    wire [2:0] O_selB;
```

```
    wire [2:0] O_selD;
```

```
    wire O_regwe;
```

```
    wire [15:0] O_imm;
```

```
    Inst_Dec uut (.I_clk(I_clk), .I_en(I_en), .I_inst(I_inst), .O_aluop(O_aluop),  
    .O_selA(O_selA), .O_selB(O_selB), .O_selD(O_selD), .O_imm(O_imm),  
    .O_regwe(O_regwe));
```

```
    initial begin
```

```
        I_clk = 0;
```

```
        I_en = 0;
```

```
        I_inst = 0;
```

```
        #10; I_inst = 16'b00010111000000100;
```

```
        #10; I_en = 1;
```

```
    end
```

```
    always #5 I_clk = ~I_clk;
```

```
endmodule
```

# Register UUT

```
`timescale 1ns/1ps

module regfile_unittest();
    reg I_clk;
    reg I_en;
    reg I_we;
    reg [2:0] I_selA;
    reg [2:0] I_selB;
    reg [2:0] I_selD;
    reg [15:0] I_dataD;

    wire [15:0] O_dataA;
    wire [15:0] O_dataB;

    reg_file uut (I_clk(I_clk), I_en(I_en), I_we(I_we), I_selA(I_selA), I_selB(I_selB), I_selD(I_selD),
    I_dataD(I_dataD), O_dataA(O_dataA), O_dataB(O_dataB));

    initial begin
        I_clk = 0;
        I_dataD = 0;
        I_en = 0;
        I_selA = 0;
        I_selB = 0;
        I_selD = 0;
        I_we = 0;

        #7; I_en = 1; I_selA = 3'b000; I_selB = 3'b001; I_selD = 3'b000; I_dataD = 16'hFFFF; I_we = 1;
        #10; I_selD = 3'b010; I_we = 0; I_dataD = 16'h2222;
        #10; I_we = 1;
        #10; I_dataD = 16'h3333;
        #10; I_selD = 3'b000; I_we = 0; I_dataD = 16'hFEED;
        #10; I_selD = 3'b100; I_dataD = 16'h4444;
        #10; I_we = 1;
        #50; I_selA = 3'b100; I_selB = 3'b100;

        #50 $stop;
    end

    always #5 I_clk = ~I_clk;

endmodule
```



# Main Test UUT

```
`timescale 1ns/1ps
```

```
// Main Testbench Module  
module main_test();
```

```
    // Variable Declarations
```

```
    reg clk;  
    reg reset;  
    reg we = 0;  
    reg [15:0] dataI = 0;  
    reg en;  
    reg [15:0] inst;  
    wire [4:0] opcode;  
    reg [15:0] addr;  
    reg en;
```

```
    wire [2:0] selA;  
    wire [2:0] selB;  
    wire [2:0] selD;  
    wire [15:0] dataA;  
    wire [15:0] dataB;  
    wire [15:0] dataD;  
    wire [4:0] aluop;  
    wire [7:0] Imm;  
    wire [15:0] dataO;  
    wire [15:0] pcO;  
    wire shldBranch;  
    wire enfetch;  
    wire endec;  
    wire enalu;  
    wire enmem;  
    wire enrgrd;  
    wire enrgwr;  
    wire regwe;  
    wire [15:0] dataResult;  
    wire O_shldBranch;  
    wire Opc;
```

```
    // Module Instantiations
```

```
    reg_file main_reg (.I_clk(clk), .I_en(en), .I_we(we), .I_selA(selA), .I_selB(selB),  
    .I_selD(selD), .I_dataD(dataD), .O_dataA(dataA), .O_dataB(dataB));
```

```
    Inst_Dec main_inst (.I_clk(clk), .I_en(en), .I_inst(inst), .O_aluop(aluop), .O_selA(selA),  
    .O_selB(selB), .O_selD(selD), .O_Imm(Imm), .O_regwe(regwe));
```

```
    alu main_alu (.I_clk(clk), .I_en(en), .I_aluop(aluop), .I_dataB(dataB), .I_Imm(Imm),  
    .O_dataResult(dataResult), .O_shldBranch(shldBranch));
```

```

cntrl_unit main_ctrl (.I_clk(clk), .I_reset(reset), .O_enfetch(enfetch),
.O_endec(endec), .O_enrgd(enrgd), .O_enalu(enalu), .O_enrgwr(enrgwr),
.O_enmem(enmem));

pc_unit pc_main (.I_clk(clk), .I_opcode(opcode), .I_pc(pcO), .O_pc(Opc));

fake_RAM main_ram (.I_clk(clk), .I_we(we), .I_addr(addr), .I_data(dataI),
.I_data(dataO));

// Opcode Assignment
assign opcode = (reset) ? 2'b00 : ((shldBranch) ? 2'b10 : ((we) ? 2'b01 : 2'b00));



// Initial and Clock Generation
initial begin
    clk = 0;
    reset = 1;
    #20;
    reset = 0;
    #25 $finish;
end

always #5 clk = ~clk;


endmodule


```

# Waveforms

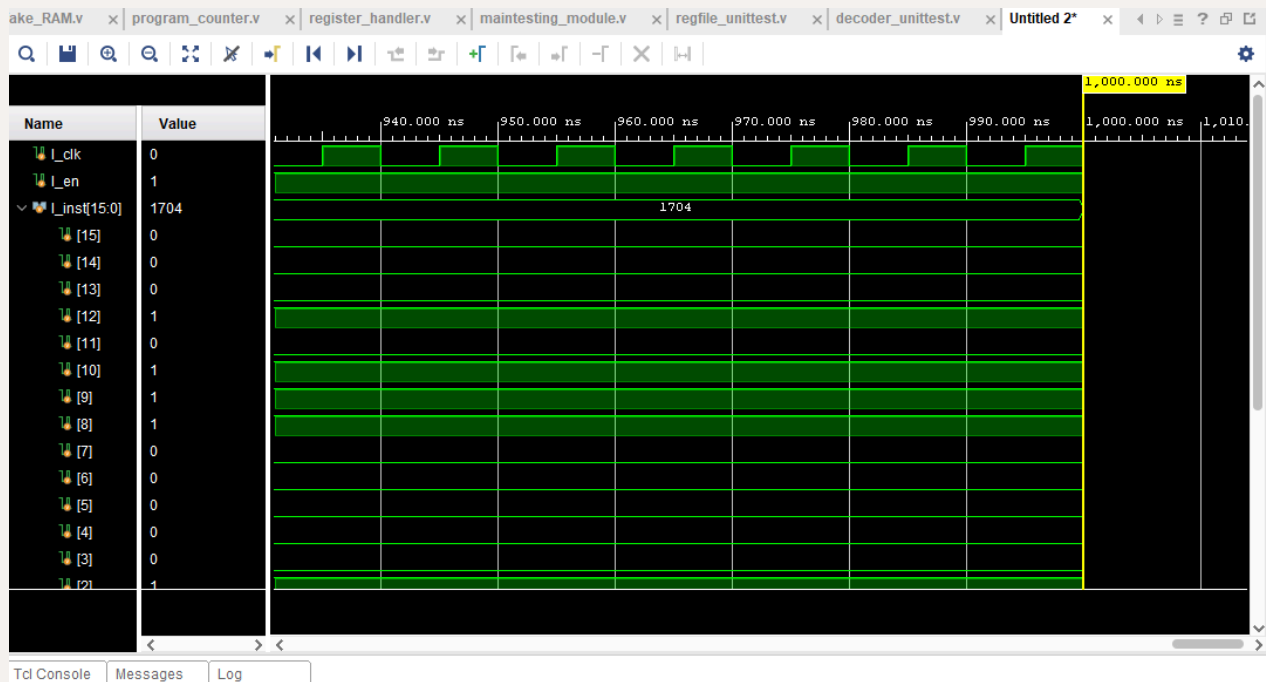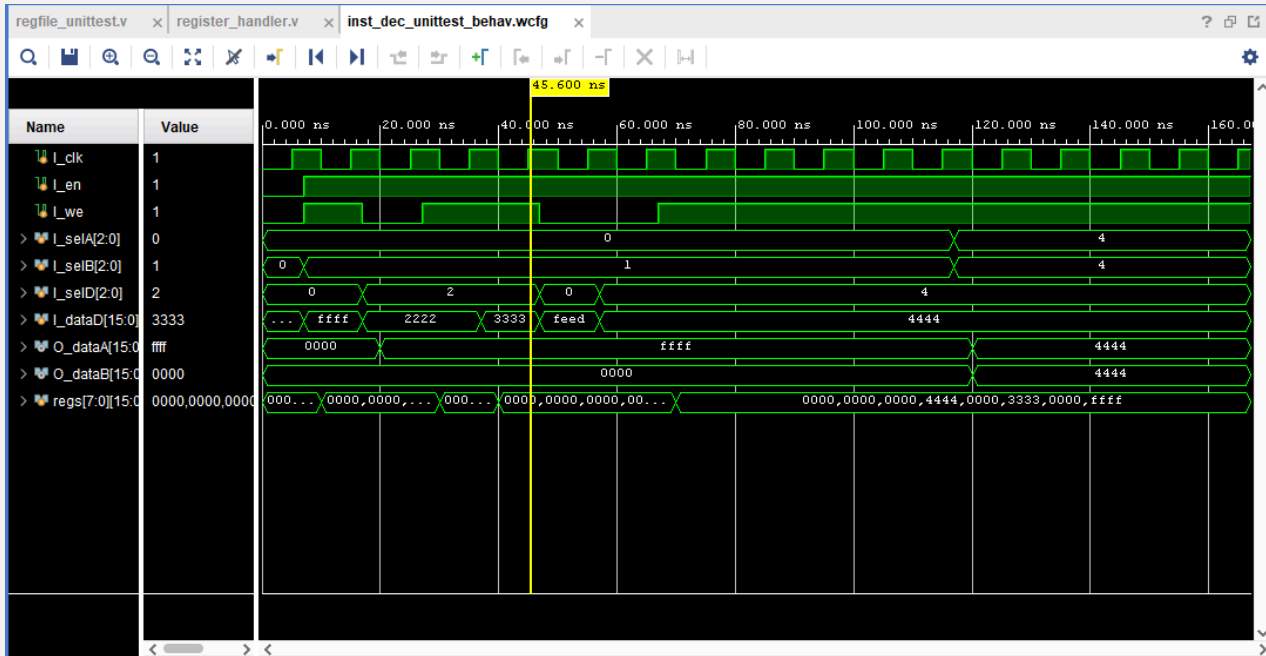

# Waveforms

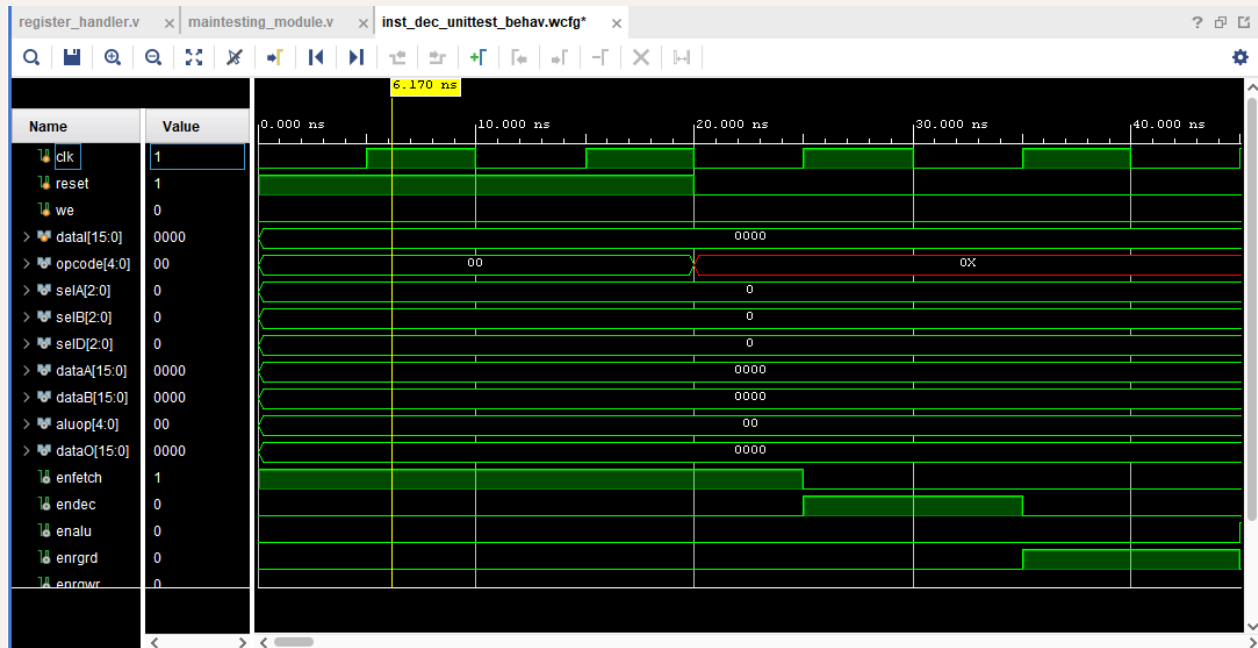

 

*Thank  
You*

